

# Kirchhoff's Rules | Procedure Of Solution Of Circuit problem

---

Kirchhoff's Law describes the [electric current](#) of a node and the voltage of a loop. These two laws form the basis of advanced circuit analysis. These laws help in the procedure of solution of circuit problems.

## Kirchhoff Current Law

The Sum of all the currents meeting at a point in the circuit is zero.

“The sum of all the currents flowing towards a point is equal to the sum of all the currents flowing away from the point”


**Mathematically**

$$\sum I = 0$$

## Convention:

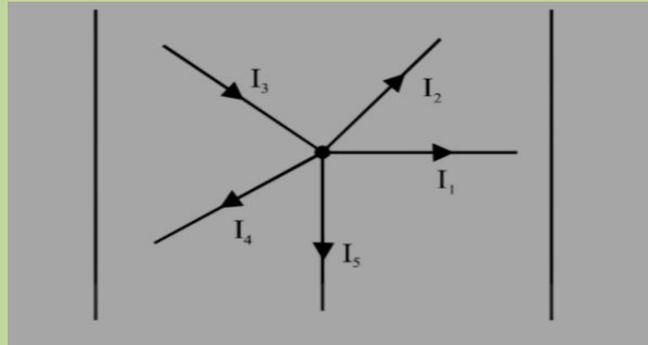- 1) The current flowing towards a point is taken, as positive
- 2) The current flowing away from a point is taken as negative

Consider four [resistances](#) meeting at point A. The current  $I_1$ , and  $I_2$  flowing towards point A are taken as +ve and current  $I_3$  and  $I_4$  flowing away from point A is taken as negative.



**Mathematically**

$$I_1 + I_2 + (-I_3) + (-I_4) = 0$$

$$I_1 + I_2 = I_3 + I_4$$

## Kirchhoff's point rule:

It is also known as Kirchhoff's point rule which verifies the law of conservation of [electric charge](#). If there is no sink or source of charge at the point, then the total charge flowing towards the point must be equal to the total charge flowing away from the point


## Kirchhoff's Voltage law:

The algebraic sum of voltage changes in a closed circuit or a loop must be equal to zero.

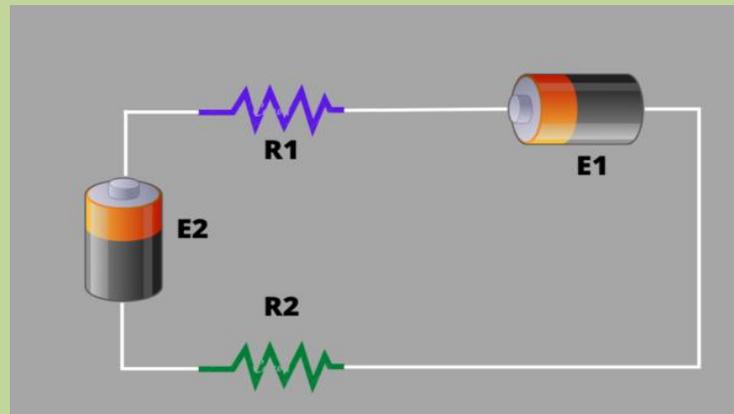**Mathematically**

$$\underline{\Sigma v = 0}$$

Consider a closed circuit  $I$  is the current which is flowing in the circuit. The direction of the current depends on the cell of a larger EMF



Let  $E_1 > E_2$  then the current flows in the anti-clockwise direction. Since the potential difference is equal to the work done on a unit positive charge or it is the gain or loss of energy when the charge is moving from one point to another point.

Thus when a positive charge  $\Delta Q$  due to the current  $I$  in the close circuit is passing through the cell  $E_1$  from low (-ve) to high (+ve) potential, work is done on it and it gains energy.

$$\text{Gain in energy} = E_1 \Delta Q$$

Similarly, when charge  $\Delta Q$  passes through the cell  $E_2$  it passes from high to low potential so it loses energy.

$$\text{Loss in energy} = -E_2 \Delta Q$$

When charge  $\Delta Q$  passes through resistor  $R_1$  it also loses energy.

$$\text{Loss in energy across } R_1 = -IR_1 \Delta Q \quad (\text{Since } V=IR,)$$

-ve sign shows that the charge is flowing from high to low potential.

Similarly, the charge also loses energy on passing through the resistor  $R_2$

$$\text{Loss in energy across } R_2 = -IR_2 \Delta Q$$

Finally, the charge reaches the negative terminal of cell  $E_1$ .

According to the law of conservation of energy, the total change in energy of the system is zero.

$$E_1 \Delta Q - E_2 \Delta Q - IR_1 \Delta Q - IR_2 \Delta Q = 0$$

$$E_1 - E_2 - IR_1 - IR_2 = 0$$

This is Kirchhoff's second rule and is simply a particular way of stating the law of conservation of energy in electrical problems.

## Rules for finding potential changes:

- The potential change is +ve if the source of 'emf' is traversed from the negative to the positive terminal, otherwise, it is negative.
- The potential change is negative if the resistor is traversed in the direction of the current, otherwise, it is positive.

## Complex Network:

***"A circuit which consists of many resistors and more than one voltage source is called a Complex Network"***

The complex circuit consists of:

### Node:

A point where two or more circuit elements

### **Essential node:**

A node where three or more circuit elements join.

### **Path:**

A trace of adjoining basic elements with no elements included more than once

### **Branch:**

The path that connects two nodes

## **Procedure Of Solution Of Circuit Problems**

- 1) Draw the circuit diagram.
- 2) The choice of loops should be such that each resistance is included at least once in the selected loop.
- 3) Assume a loop current in each loop, all the loop currents should be in the same sense. It may be either clockwise or anti-clockwise.
- 4) Write a loop equation for all the loops.
- 5) For each loop equation, just follow the rules.
- 6) Solve these equations for unknown quantities.